

Peer-graded Assignment: Peer Assignment: Light an LED

Submit by Oct 19, 2:59 PM +08

Submit your assignment soon

Even though your assignment is due on Oct 19, 2:59 PM +08, try to submit it 1 or 2 days early if you can. Submitting early gives you a better chance of getting the peer reviews you need in time.

Instructions

My submission

Project Title *

Give your project a descriptive title

Build a circuit that lights an LED when it is sufficiently dark in a room. Demonstrate the circuit by covering the photoresistor to simulate darkness.

Create a video (or a screencast) of your circuit in action.

If you have real hardware then demonstrate the real circuit. If you do not have real hardware then use the simulator.

Regardless of which method you use, provide a link to the location of your video or screencast on the Internet. Do not upload your video here.

URL

